

14 August 2005

## Radiotron Designer's Handbook

I've been asked to provide some reference works on the cathode-follower output stage. This isn't easy to do, as very little has been written on the topic. Even the expansive and exhaustive *Radiotron Designer's Handbook* is startlingly thin and terse on this topic. Here is all Langford-Smith has to say about amplifiers sporting cathode-follower output stages:

### SECTION 9: CATHODE-FOLLOWER POWER AMPLIFIERS

The principles of cathode followers have been covered in Chapter 7 Sect. 2(i). A cathode follower may be used either as driver for a Class B - AB2 stage, or as the output stage itself.

A cathode follower forms almost an ideal driver stage, having very low plate resistance and distortion, although it requires a high input voltage. It is commonly used, either singly or in push-pull, in high power a-f amplifiers where the distortion must be reduced as much as possible. If parallel-feed is used, the hum is reduced by the factor  $1/(\mu + 1)$ ; see Chapter 7 Sect. 2(ix) Case 4. A cathode follower driver stabilizes the a-f signal voltage, but does not stabilize the grid bias.


Cathode follower output stages introduce serious problems, and are not suitable for general use. The difficulty is in the high input voltage which is beyond the capabilities of a resistance-coupled stage operating on the same plate supply voltage. Two methods are practicable, either a step-up transformer in the plate circuit of a general purpose triode, or a resistance-coupled amplifier with a plate supply voltage about 3 times the plate-cathode voltage of the cathode follower. In order to take advantage of the low distortion of the cathode follower, the preceding stage should also have low distortion. A general purpose triode is to be preferred to a pentode or high- $\mu$  triode with resistance coupling, and it may have an unbypassed cathode resistor.

One practical amplifier which has been described in the literature (Ref. F3) uses 700 volts supply voltage to the 6SN7 penultimate stage and eight 6V6-GT valves in push-pull parallel operation in the cathode follower output stage. Negative feedback is used from the secondary of the output transformer, and the damping on the loud speaker is as high as practicable. However, the total harmonic distortion at 50 c/s is over 1% at 8 watts output, and 1.7% at 20 watts. The high output voltage which must be delivered by the resistance-coupled penultimate stage thus shows its effect on the distortion, even though the plate supply voltage has been increased to a dangerously high value.

It's all true enough, but I wish he had written "even though their low output impedance and low distortion appear attractive," as  $r_p$  isn't the same as  $Z_o$ . Moreover, I would argue that he isn't altogether right about the cathode-follower output stage not stabilizing the grid bias, as all output transformers hold primaries with relatively high DCR, which acts as a simple cathode-bias resistor and makes even a fixed-biased cathode-follower output stage, a quasi-cathode-biased one. For example, where a fixed-bias, EL34-based amplifier might need  $-35V$  to set the output tubes' idle current, those same EL34s in a cathode follower output stage amplifier might only require  $-15V$  to set the same idle current, as the primary's wire resistance acts as a cathode resistor that displaces 20 volts.

And while I must agree that the cathode-follower output stage makes huge demands on its driver stage, I believe that we can extract all that is desirable from this topology without introducing further problems—if we are both careful and clever, that is. For example, as was mentioned in the last blog entry, solid-

# Tube CAD

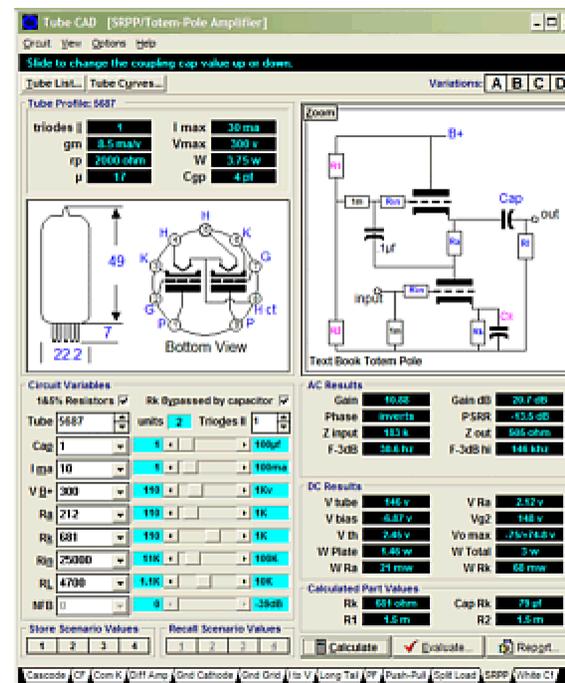

## Tube CAD does the hard math for you.

This program covers 13 types of tube circuits, each one divided into four variations: 52 circuits in all. Tube CAD calculates the noteworthy results, such as gain, phase, output impedance, low frequency cutoff, PSRR, bias voltage, plate and load resistor heat dissipations. Which tube gives the most gain? Tube CAD's scenario comparison feature shows which tube wins.

Windows 95/98/Me/NT/2000/XP

For more information, please visit our Web site :

[www.glass-ware.com](http://www.glass-ware.com)


To purchase, please visit Antique Electronic Sales' website:

state rectifiers make adding extra power supply rails easy, which wasn't true when the *Radiotron* was written. These added power supply rail voltage can be negative or a multiple of the main B+ voltage. In either case, the increased usable voltage can be put to good use.
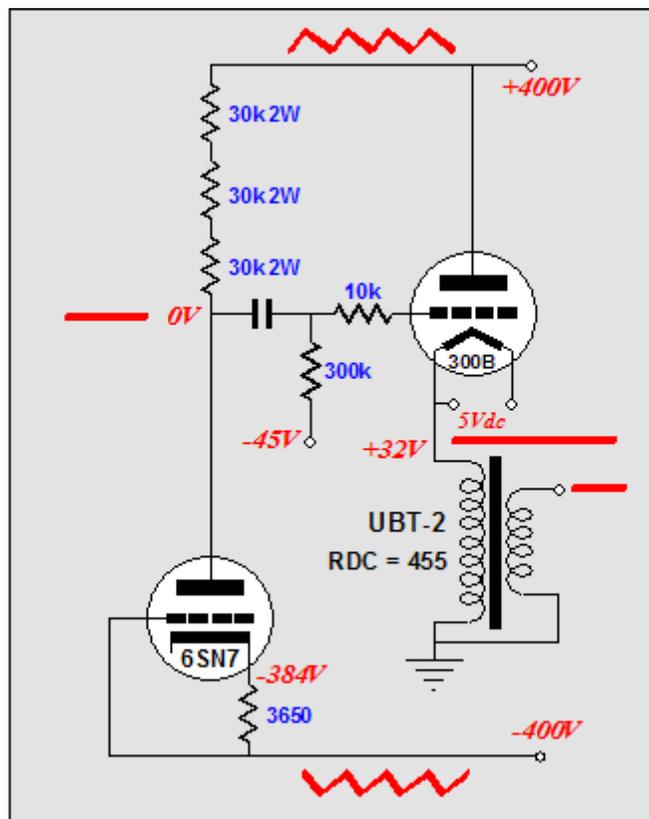
### Common-cathode amplifiers


Last time, we looked at a few possible bipolar power supply circuits. Common to each circuit was a common-cathode amplifier used as the input stage. Why? This topology allowed us to interject the negative power supply rail noise into the common-cathode's output. Why do that? The driver stage is referenced to the negative rail, not ground, which can lead to power supply noise problems.

Since the driver stage spans the negative to the positive rail, it has twice the voltage available to it than does the output stage, which allows for the needed big voltage swings, but it also adds the problem of power-supply noise spilling into the output. The output stage itself rejects much of the B+ noise at its plate; however, if the power-supply noise is presented to its grid, then it will be relayed along with the music to the loudspeaker. Now in this bipolar power supply amplifier, if the driver tube and its cathode resistor's combined effective impedance equals that of its plate load resistance, the noise will null at the driver stage's output, as the positive rail noise is out of phase with the negative rail's noise. This desired condition is met when the plate resistor equals  $(\mu + 1)R_k + r_p$ , with the cathode resistor left unbypassed.



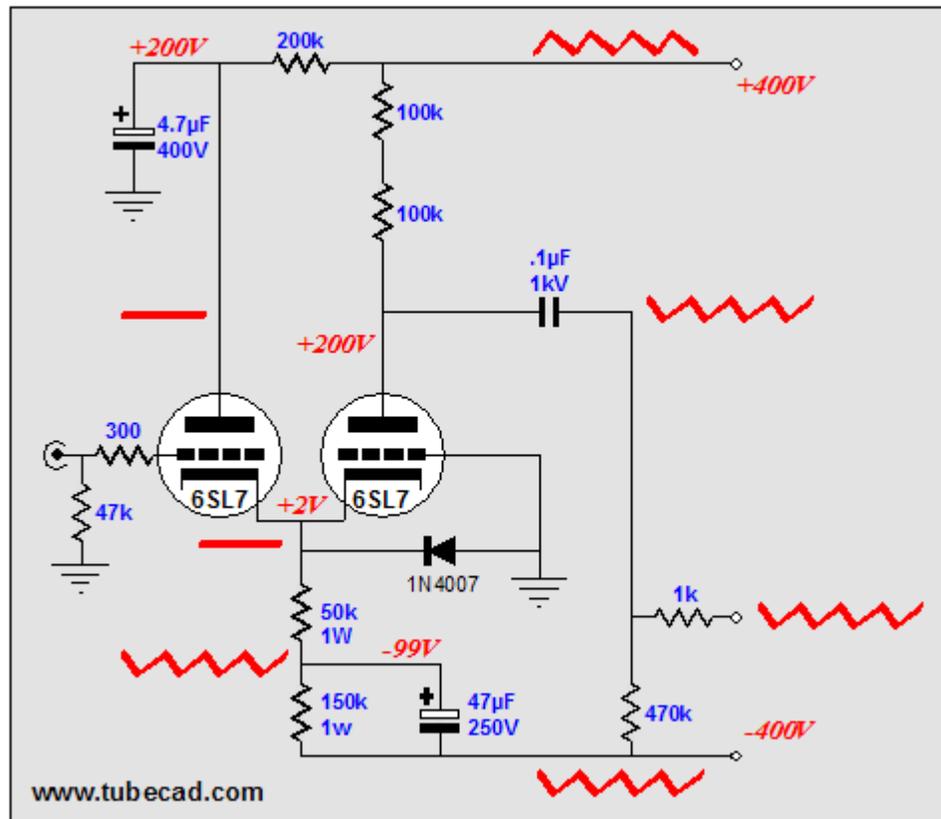Well, it will null if the driver stage's grid is terminated into the negative rail; otherwise the power supply noise will leak through or, worse, be amplified. Imagine that the grid is "grounded" to ground via a coupling capacitor. In such a







Is the common-cathode amplifier the only topology that allows us to inject the negative power supply rail noise into its output? No, as several other topologies can be “fixed” to achieve the same end, starting with the insanely ubiquitous grounded-cathode amplifier. (Imagine that this topology were made illegal; what would 90% of tube gurus do?)

What’s wrong with the grounded-cathode amplifier? Nothing. Nor, however, is there anything right about it, in an absolute context, as such an evaluation makes zero sense from the absolute point of view; absolute means entirely independent of loads, power supplies, and input impedances. No circuit is either good or bad outside of a context, a larger super-circuit or system that allows evaluations to be made. Which is better: two or seven years? “It depends,” is the only possible answer. *Two years* is better if you face sentencing for a crime you committed, but *seven years* is better if you are diagnosed with cancer.

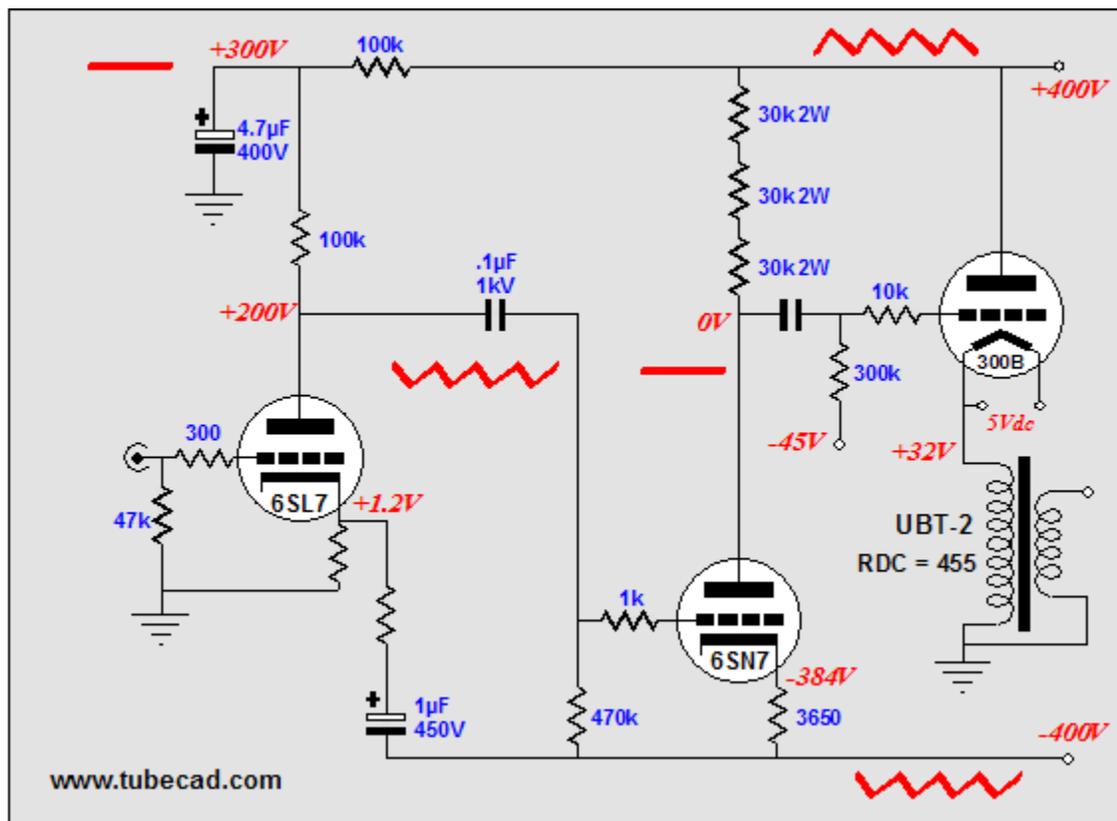So how do we superimpose the negative power supply rail noise on a grounded-cathode amplifier output? We can inject a sampling of the negative rail noise into the cathode, as this input does not invert the input signal at the plate. In the schematic below, we see one possible technique.



Alternatively, we could use a cascode input stage. Normally, the cascode is rightly viewed as having an appallingly low PSRR figure—in fact, virtually none. But in the totality of the entire amplifier circuit, this liability becomes an asset. All we have to do to exploit the cascode's poor PSRR figure is terminate its plate resistor into the negative rail, not the positive B+ nor ground. As shown below, almost all of the negative rail noise will appear at the cascode's output.

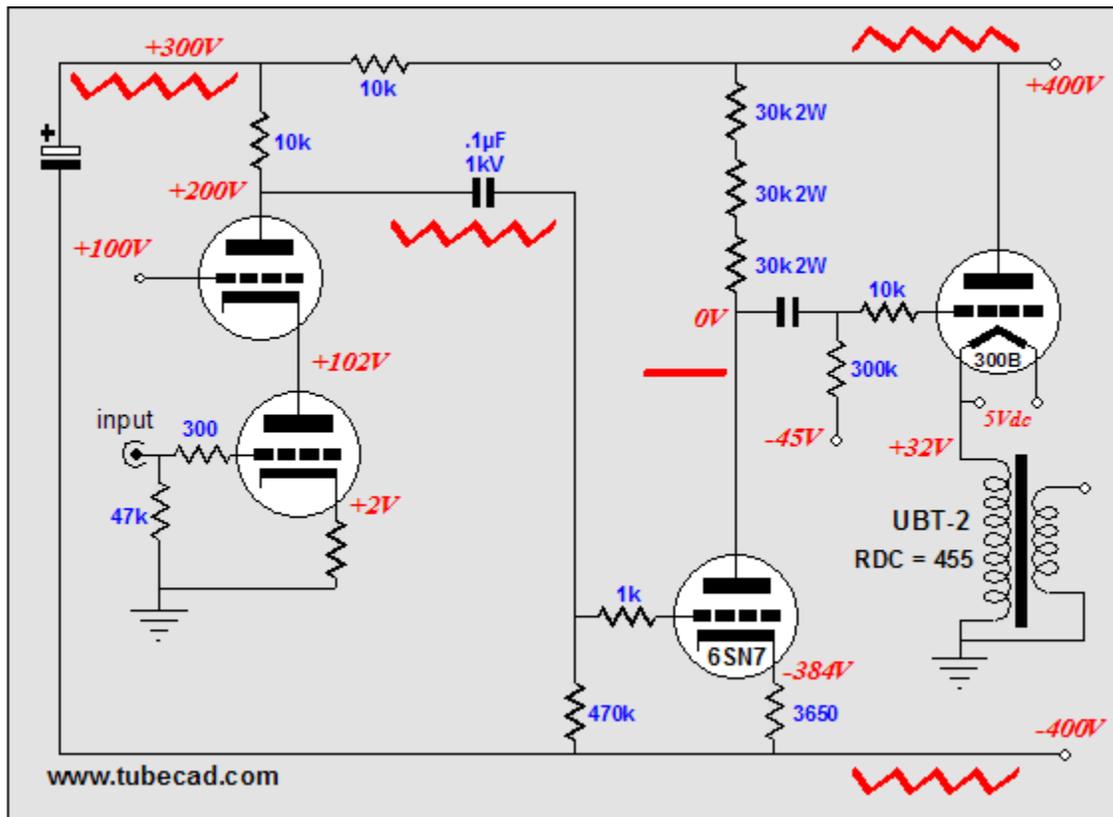

Using a pentode-based input stage, with the same power supply decoupling, would also yield the desired result.

One practical problem all of the topologies will face is that the negative power supply rail will not be taxed nearly as much as the positive rail will be, as the positive rail must feed the input, driver, and output stages; while the negative rail will only feed the first two. In other words, we can reasonably expect more noise on the positive than the negative power supply rail. Thus, some tweaking will be needed; for example, smaller filtering capacitors on the negative rail.

### Next time

I wanted to post about twice as much today, but the day proved shorted than I had counted on. The next blog entry will cover mono-polar power supply input and driver circuits.

//JRB

[< Back](#)

www.tubecad.com

Copyright © 1999-200 4 GlassWare

All Rights Reserved

[Next >](#)