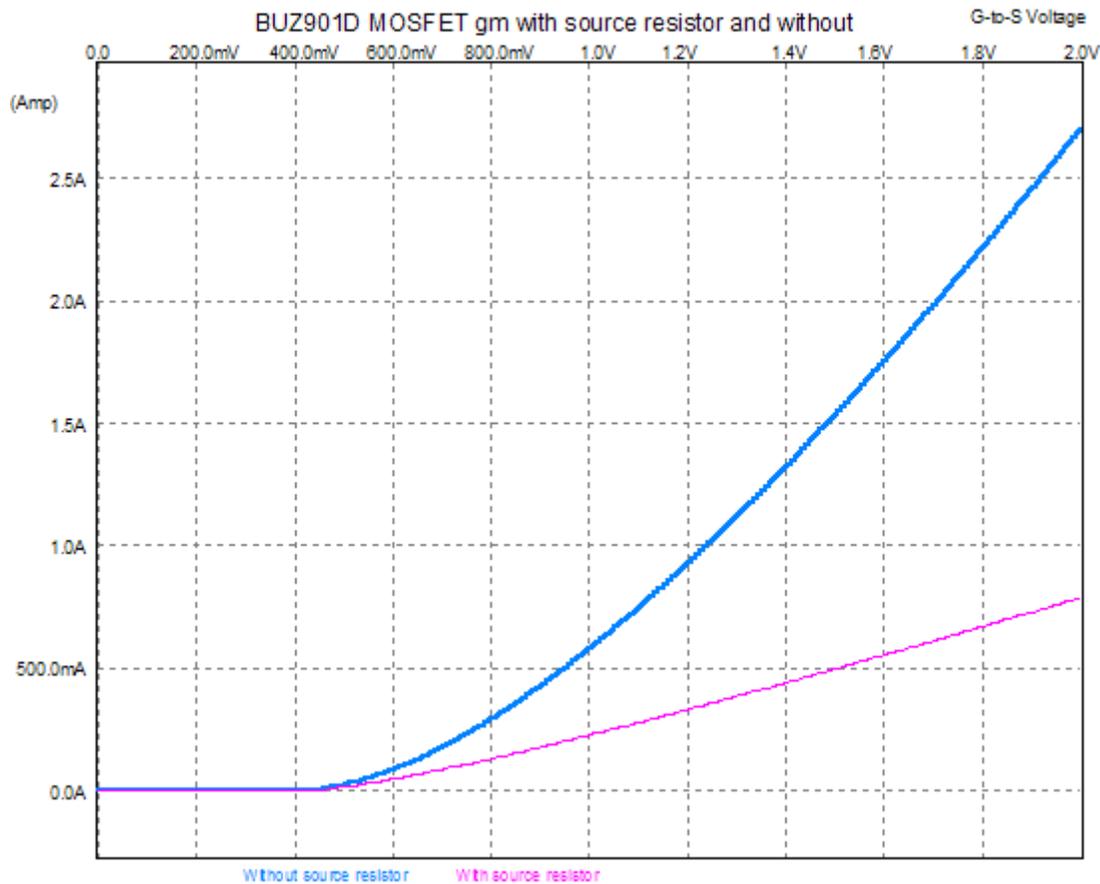


$$A = -\mu R_a / [R_a + r_p + (\mu + 1)R_k]$$

If this signal at the cathode exactly equaled the input signal in all but amplitude, then the distortion would vanish from the plate, as the tube would have to have produced zero distortion to create such equality. Real tubes do distort and that distortion is present on the unbypassed cathode resistor. This distortion is in voltage anti-phase with the input signal. For example, if the cathode voltage is too low compared to the grid's voltage, the tube will increase its conduction, which will lift the cathode voltage. On the other hand, if the cathode voltage is too high compared to the grid's voltage, the tube will decrease its conduction, which will drop the cathode voltage. In other words, feedback. The larger the cathode resistor's value, the more feedback.

Below is a graph of a power MOSFET with and without a source resistor (1 ohm). Note how much transconductance (gm) was lost (hold a ruler to the screen) and how much more linear the transfer curve is. The unbypassed resistor produced a good amount of feedback, but at the cost of gm.



The formula for the decrease in a MOSFET's gm because of an unbypassed source resistor is:



$$g_m' = g_m / (1 + g_m R_s)$$

A triode's decrease in gm because of an unbypassed cathode resistor is:

$$g_m' = \mu / (r_p + [\mu + 1]R_k)$$

Wait a minute

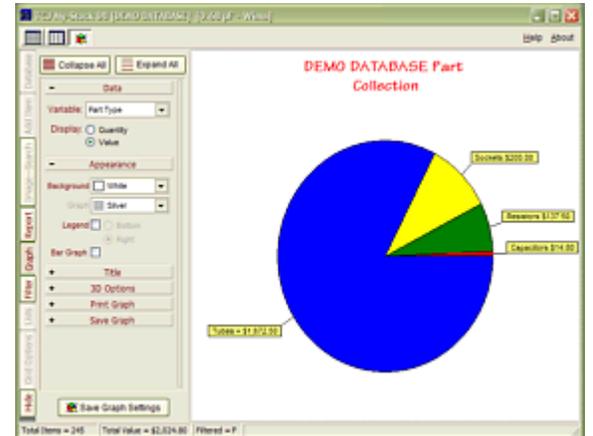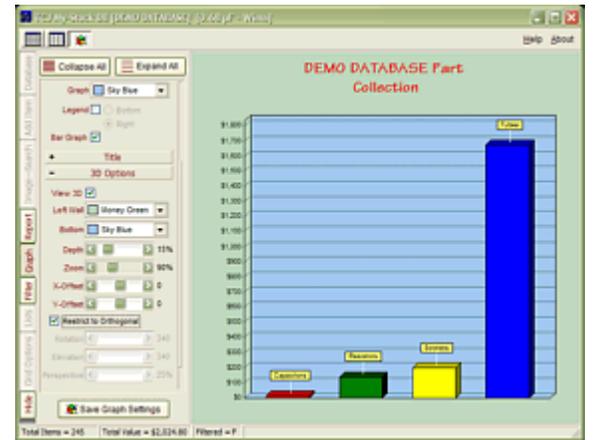You mean to tell me that the greatest minds (and ears) in tube world voted for the circuit with the most feedback? It is almost as if country-western singers were polled and the result was that most found sobriety preferable to




Part Type	Name	Quantity	Brand	Vendor
Tube	2A3	3	RCA	Electronic Parts
Tube	6SL7	4	Sylvania	Swag Me
Tube	6812	4	Sylvania	Jera's TV & S
Tube	6SL7	11	Tung-Sol	Jera's TV & S
Tube	6SL7	3	Deflection	Free Mart
Tube	6SL7	18	Sylvania	Free Mart
Tube	12AT7	22	National	Swag Me
Tube	5687	6	Tung-Sol	Swag Me
Tube	6BD6A	4	GE	Antique Electron
Tube	5891	3	RCA	Swag Me
Tube	6L84	5	Mullard	Swag Me

TCJ My-Stock DB helps you know just what you have, what it looks like, where it is, what it will be used for, and what it's worth. TCJ My-Stock DB helps you to keep track of your heap of electronic parts. More details.

Version 2 Improvements


- List all of your parts in one DB.
- Add part Images.
- One-click web searches for information.
- Vertical and horizontal grids.*
- Create reports as PDFs.*
- Graphs added 2D/3D: pie & bar.*
- More powerful DB search.
- Help system added.
- Editable drop-down lists for location, projects, brands, styles, vendors and more.

*User definable

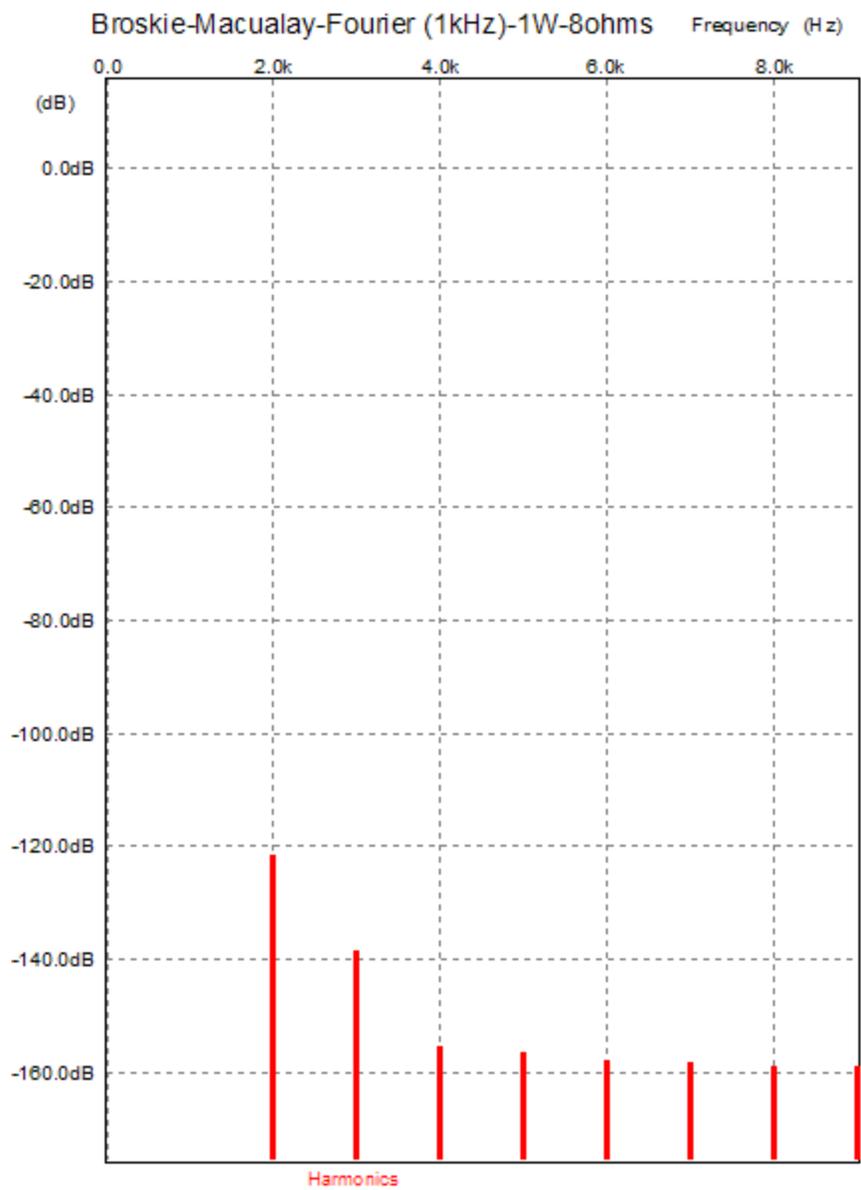

Further enhancements

I cannot let a schematic sit five minutes before wanting to improve it. In this case, the power supply is probably the weakest link, as it is not regulated. Regulating the power supply is one possibility, but an easier, less expensive tact is to regulate only the OpAmp's power supply. However, we cannot afford to lose a precious volt of output swing from the OpAmps and cascading a regulator from the existing power supply will lose at least 3-volts potential swing, because of the voltage drop across the regulator.

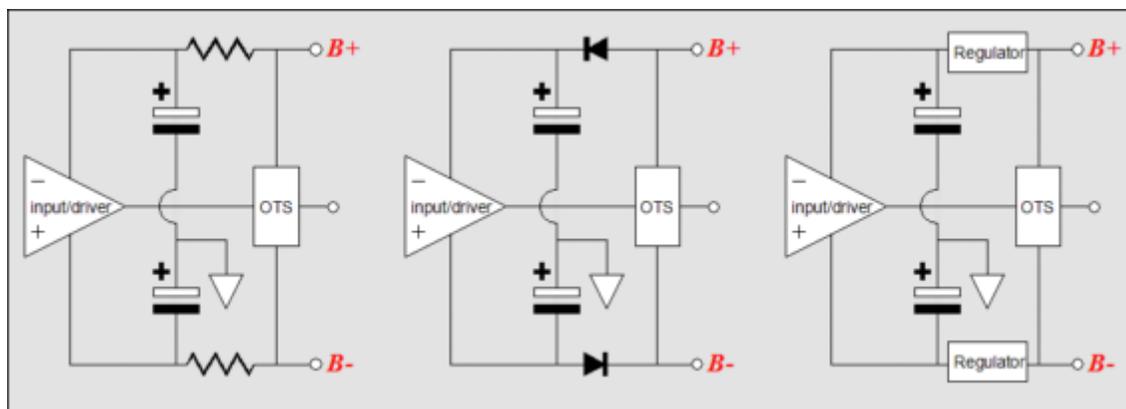

7 watts?

Why not build a 30 or 100 watt version? Theoretically such an amplifier is possible, but finding suitable OpAmps to drive it is challenging. In spite of there being thousands of OpAmps, only a few sound all that good and very few can handle 50-volt rails, which a 100W amplifier would require. I know that Apex make high-voltage OpAmps, but I have no practical experience with them. If you have a suggested OpAmp, please send it in.

//JRB

[< Back](#)

www.tubecad.com

Copyright © 1999-2005 GlassWare

All Rights Reserved

[Next >](#)