

## Low Dissipation SE Class-A?


28 January 2005

Support the Tube CAD Journal

Only \$29

TCJ Push-Pull Calculator

Version 2

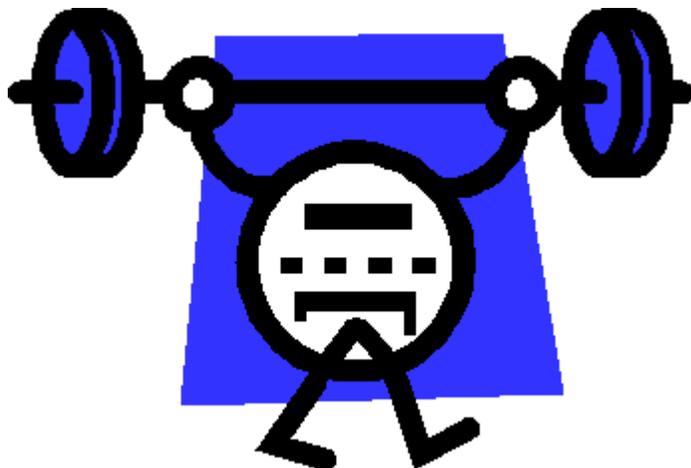

### Taylor source follower on steroids

I have just broken the unspoken, but well understood rule: always mention tubes in the title. Not to fear, tubes are on their way, but first we must go through the steps.

First of all, I am a little fearful to describe any circuit that can be exploited by a marketing department. Hype sells and today's hot audio-gear adjectives include "single ended" and "class-A." Unfortunately (at least for marketing and finance departments), these adjectives unavoidably necessitate low efficiency and high heat dissipation. The only problem with big, heavy, inefficient, and expensive is that is big, heavy, inefficient, and expensive. What if it were otherwise? What if a small, light, efficient, and cheap class-A, single-ended, amplifier could be made?

Well, until the laws of physics get amended or revoked, the engineering department will have its hands tied; on the other hand, the marketing department is not so constrained, as long as the circuit is odd or complex enough to confuse most audiophiles, then generous loopholes are waiting to be exploited.


### A quick aside

I remember once being told by a stereo salesman that the one loudspeaker's tweeter was radically better than all other tweeters. "How so," I asked. "The sound travels faster to your ear from this tweeter than it would from other tweeters," was the answer. You guessed it: that is why it sounded so fast.


While on the topic of foolish audio sales people, I was surprised by the number of clowns running demonstrations of disgustingly expensive audio equipment at the CES show I attended recently. Back in the old days, when stereo sales were soaring, say 1979, it was common to walk into a stereo store that placed all the electronics on the back wall and all the speakers against the front wall. You would sit and listen away as the salesman would control which amplifier and loudspeakers you heard. Regrettably, a few salesmen were content to leave at that; instead, they would ride the volume control as you listened. The result was SpecTacUlaR, as the bass rumbled just to the point of breakup on the first notes of Richard Strauss's Also Sprach Zarathustra and then the volume would relapse into sane levels as the trumpets began to sound (when the 50% distortion would be more noticeable). The first time I discovered that this was happening, I turned around and asked what the salesman was doing. He looked at me in a puzzled way






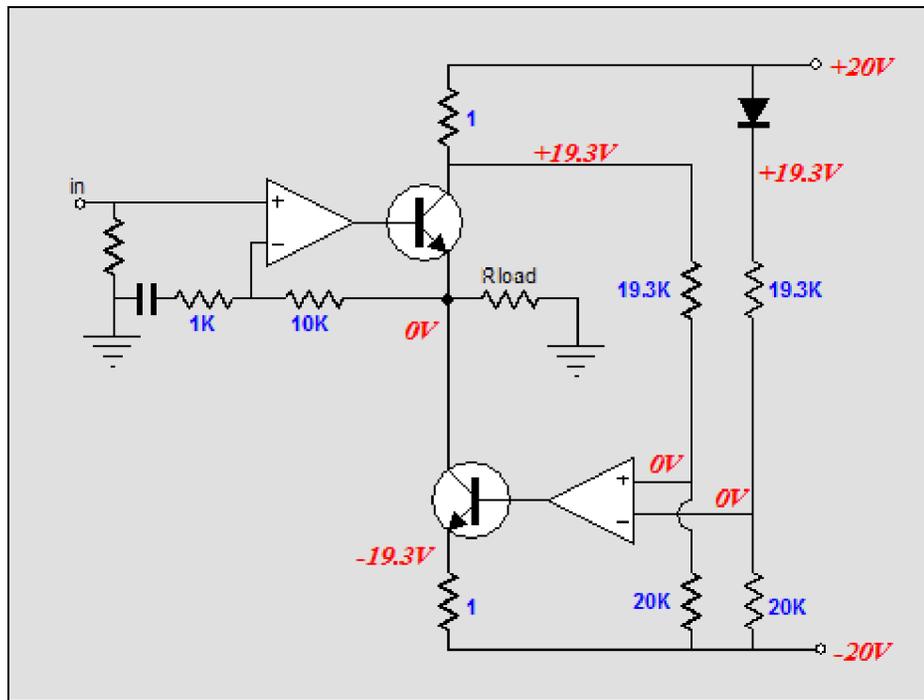
the schematic typo was ever caught. I'm sure many readers are still scratching their heads over even this corrected schematic. Just what is going on here? Well, below is a simplified version of the amplifier.



At idle, the amplifier maintains a steady bias current through the output transistors, as the bottom OpAmp strives to keep its inputs at the same voltage level, which is only possible when the voltage drop across the top 1-ohm resistor equals that across the diode. Or, if you wish to adjust freely the idle current, then the schematic below displays how this can be accomplished, although the idle current will drift with the rail voltages, whereas the diode (or any voltage reference) will maintain a constant idle current. In this example, the idle current has been set to 100mA,  $0.1V/1\text{ ohm}$  equals 100mA.

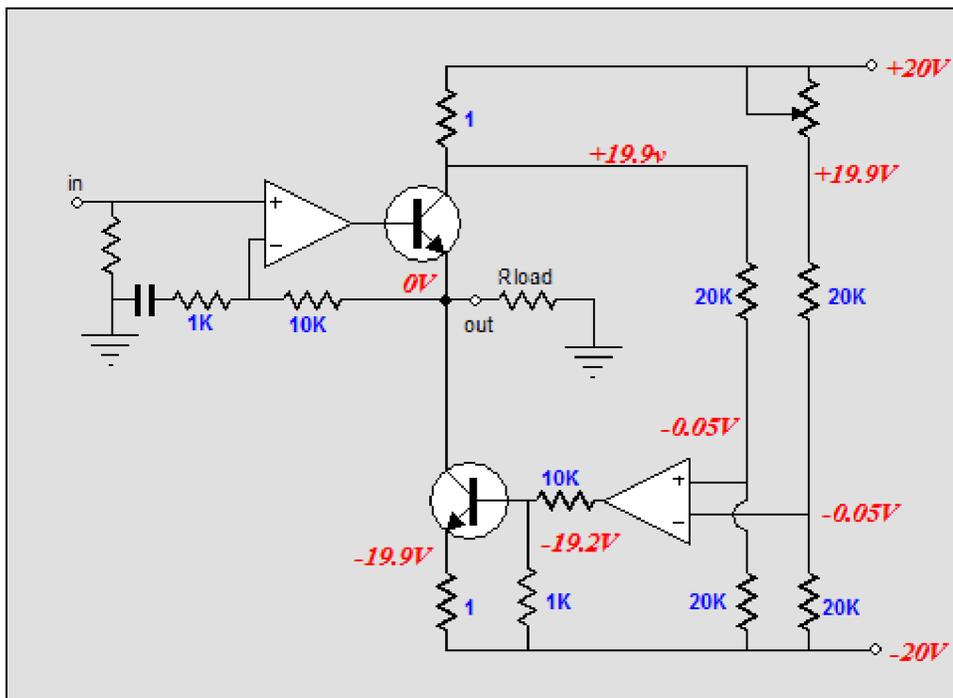

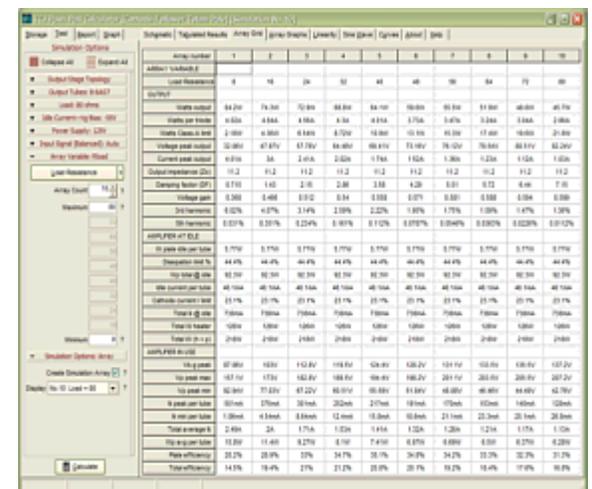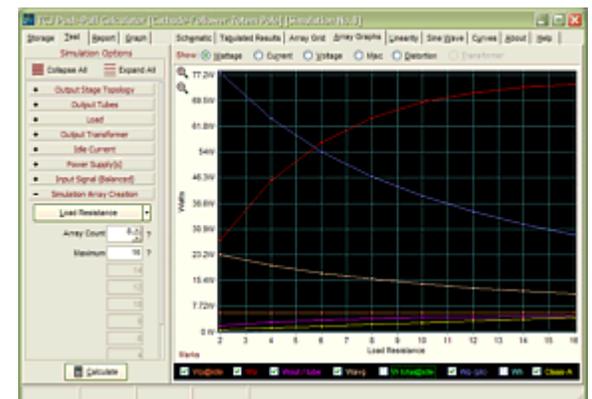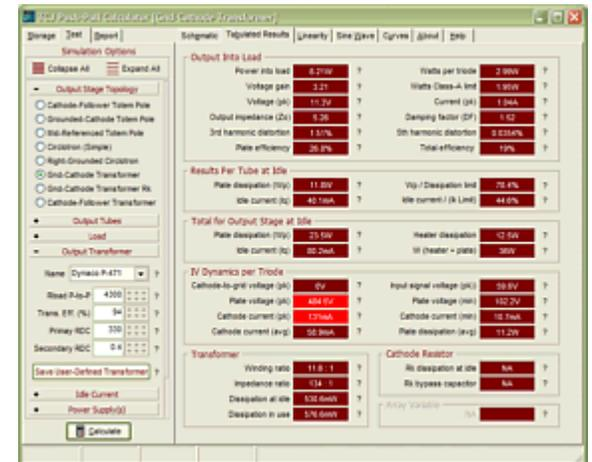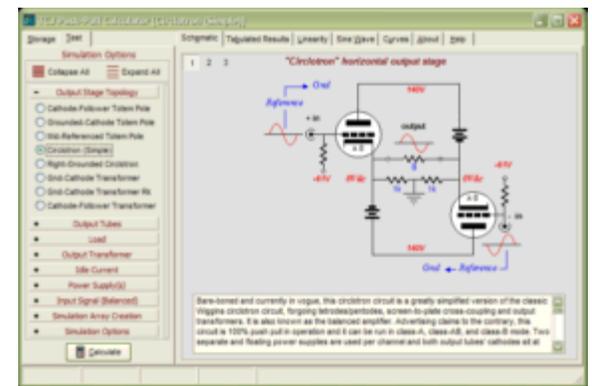
How does the amplifier work? Basically, it the White cathode follower (Taylor circuit) all over again. The flow of current through the top output device controls the flow of current through the bottom output device. When the input signal





swings positive, the voltage drop across the top 1-ohm resistor increases, which is relayed as a negative pulse to the OpAmp's non-inverting input, which in turn triggers a large negative swing of its output, which shuts off the bottom output device's conduction, as the OpAmp can only decrease the bottom output device's conduction from 100mA down to zero. Once the 100mA is used up, it's class-AB all the way—well, at least as far as the bottom output device is concerned. The top output device, on the other hand, never stops conducting, as it hits the strictly imposed 100mA limit.

For example, if the input signal swings negative, the voltage drop across the top 1-ohm resistor decreases, which is relayed as a positive pulse to the OpAmp's non-inverting input, which in turn triggers a positive swing of its output, which furthers the bottom output device's conduction, which allows it to cope with the bottom half of the waveform. But the top output device can never conduct less than 100mA, as the OpAmp will always counter any dip below 100mA with an increase in conduction of the bottom tot device to force the top device to conduct at least 100mA.

What purpose is served by the other set of resistors that bridge the positive and negative power supply rails, whose nexus connects to OpAmp's negative input? They serve two purposes: they sidestep the power supply noise and the rails' collapsing voltage under heavy use (in a real class-A amplifier, heavy use does not collapse the rail voltages; just as for a Marine, war does not over tax him, as he was already over taxed). Clever, no? Yes, indeed and Mr. Macaulay well earned his prize, but is it really class-A? Is it really single ended?

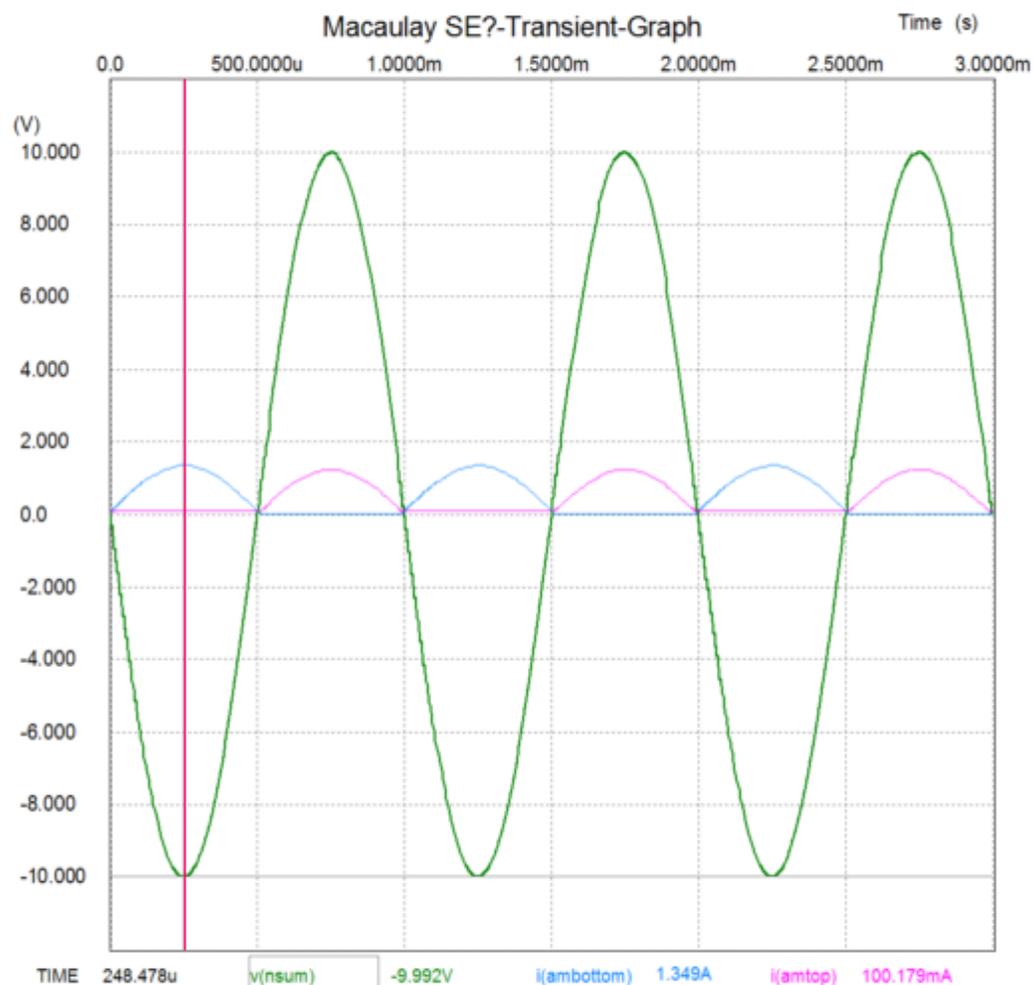

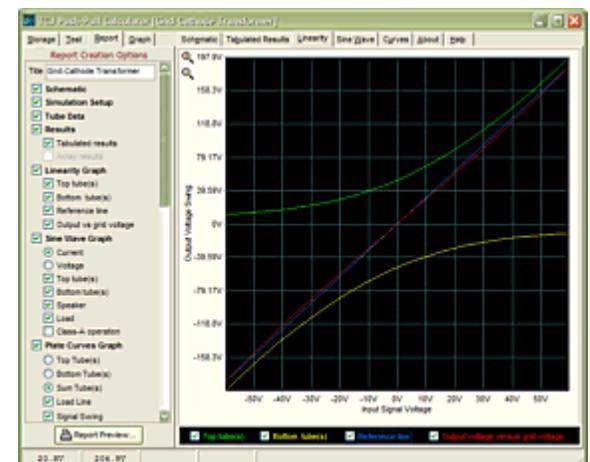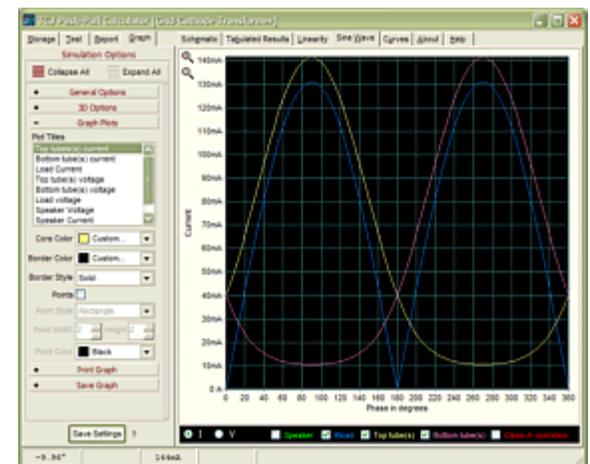If a thousand EE professors were shown the graph above, How many would immediately think: single-ended class-A? "But as least one output device always conducts—see how the red line never touches the zero line—so we can advertise it



## TCJ PPC Version 2 Improvements

- Rebuilt simulation engine
- Create reports as PDFs\*
- More Graphs 2D/3D\*
- Help system added
- Target idle current feature
- Redesigned array creation
- Transformer primary & secondary
- RDC inclusion
- Save user-defined transformer definitions
- Enhanced result display
- Added array result grid

\*User definable

TCJ Push-Pull Calculator has but a single purpose: to evaluate tube-based output stages by simulating eight topologies' (five OTL and three transformer-coupled) actual performance with a specified tube, power supply and bias voltage, and load impedance. The accuracy of the simulation depends on the accuracy of the tube models used and the tube math model is the same True Curves™ model used in GlassWare's SE Amp CAD and Live Curves programs, which is far more accurate than the usual SPICE tube model.

Download or CD ROM  
Windows 95/98/Me/NT/2000/XP









[< Back](#)

www.tubecad.com

Copyright © 1999-2005 GlassWare

All Rights Reserved

[Next >](#)