

Big Amplifiers

19 March 2005

Big amplifiers

While at the CES in January, I was surprised to find so many gargantuan tube amplifiers: huge, massive, expensive amplifiers, many the size of small refrigerators or big air conditioners. These amplifiers held more glass than my wallet could bear to contemplate. The motives are obvious: these days power and overindulgence are both desired and marketable. I have to admit that I was ambivalent: on one hand, I was impressed by the audacity of the amplifiers and I do appreciate what such a powerful amplifier can bring to a large-orchestra composition, such as any of Mahler's later symphonies. On the other hand, I was disappointed to see the more-must-be-better philosophy win. (Have you ever noticed how easily many over compensate: the bald man who buys a toupee the size of a dead opossum, the A-cup woman who moves up to double D. Imagine if he had bought the smallest, thinnest toupee made, which only partially covered his scalp, no one would guess that he was wearing a rug. Or, imagine if she had stopped at a B cup, no one would know that she had visited a surgeon.)

Beyond philosophical objections to big for the sake of big, big amplifiers face a few design hurdles. For example, high-wattage MOSFETs and transistors are much poorer performers than comparable low-wattage devices. And with tube amplifiers, big output transformers seldom sound as good as small transformers to my ears. (I own pairs of the big Tango 120 watters and Heathkit WM-6s.)

Why? I am not exactly sure. My guess is that the small output transformer holds a higher ratio of copper to iron. Or, maybe that the small transformer is easier to make well because of its smaller coil bobbin. But if I had to place a bet, it would be on the output transformer bringing its own distortion in the form of magnetic hysteresis in the core, which is most notable in the smallest signals; and with big output transformers, the small signal becomes too large, requiring large output

Support the Tube CAD Journal

Only \$19.95
to keep track of your
tube and part collection

TCJ My-Stock DB

swings to overwhelm. Of course, if your loudspeakers are highly inefficient, then you have taken a giant step sideways by moving up to a big amplifier.


Single-ended amplifiers *do not* suffer from this problem, as the output transformer's core is always magnetized in one direction that never reverses, so this hysteresis effect is never encountered. This probably explains why horn loudspeakers work so well with single ended amplifiers, as they work with just a few tenths of a volt of signal (additionally, most horn-loaded speakers exhibit a good deal of 2nd harmonic distortion due to the compression chamber not exactly matching the horns input impedance, which if phased correctly, can be largely undone by the single-ended amplifier's counter-balancing distortion).

Still, there are times when a big amplifier is the only amplifier that will work in a system and I do believe in lots of headroom.

Design example: four Dynaco ST-70s

Working on the assumption that more is always better, you pick up that extra Dynaco ST-70 at a garage sale, bring your collection of ST-70s up four. Now, what are you going to do with it? Of course you could sell it, but since you already own three ST-70s this is not likely. More likely, you imagine that you will build a super pair of amplifiers out of the four. You reason that since one ST-70 puts out 35 watts per channel, four will put out 140 watts per channel. Now we are talking real power. The question that remains is, How are four stereo amplifiers made into one?

The easiest answer is to cascade enough cable splitters to feed four ST-70 sub amplifiers through one channel's signal and then strap all four outputs together. Will this work? Yes and no. if your speakers are 2 ohm, yes; if 8 ohm, no. The Dynaco ST-70's output transformer, the P-431, holds a primary impedance of 4300 ohms, when the 8-ohm tap is loaded with an 8-ohm load. And since the four output transformers are in parallel, the winding ratio remains constant, so the same 4300 ohms is reflected with the 8-ohm load.

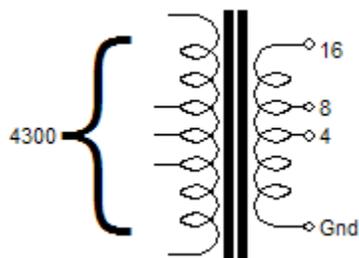

A 4300-ohm load, however, is not what eight EL34s need to see to put out 140 watts. Remember that four times the watts into the same load means twice the output voltage, but the output tubes must follow the same plate-voltage swings as before. In other words, because we have quadrupled the number of output tubes, we must quarter the plate-to-plate impedance. In other words, in order for eight EL34s to put out 140 watts, they need to see a plate-to-plate load of $4300/4$, or 1075 ohms. One solution is to use a 2-ohm load across the 8-ohm tap




The screenshot shows a table of items in the database. The table has columns for Name, Type, Brand, Group, Style, Vendor, Project, Quantity, Condition, Value, Part, Total Value, Stock, Location, and Comments. The items listed are RCA 5691 tubes. The table is filtered by "F".

Name	Type	Brand	Group	Style	Vendor	Project	Quantity	Condition	Value	Part	Total Value	Stock	Location	Comments
5691	Tube	RCA	Triode	9-Pin Min.	Antique Electronic Supply	Line Amplifier	4	NOS	\$6.50	\$26.00	\$26.00	Keep	Box 3	Tested
5691	Tube	RCA	Triode	9-Pin Min.	Antique Electronic Supply	No Project	3	NOS	\$50.00	\$150.00	\$150.00	Keep	Box 3	Nice tube, should see what they are going for on ebay
5691	Tube	RCA	Triode	9-Pin Min.	Antique Electronic Supply	Power Amplifier	5	NOS	\$20.00	\$100.00	\$100.00	Keep	Box 1	Might be worth a bit more!

and ground, as this impedance against the output transformer's impedance ratio (the winding ratio squared) equals 1075 ohms. Another solution is to attach 4-ohm loudspeakers across the 16-ohm tap and ground, as this impedance will reflect down to 1075 ohms. What if you don't own 4-ohm loudspeakers? The only answer is to reconfigure the secondaries, so that an 8-ohm load reflects down output 1075 ohms.


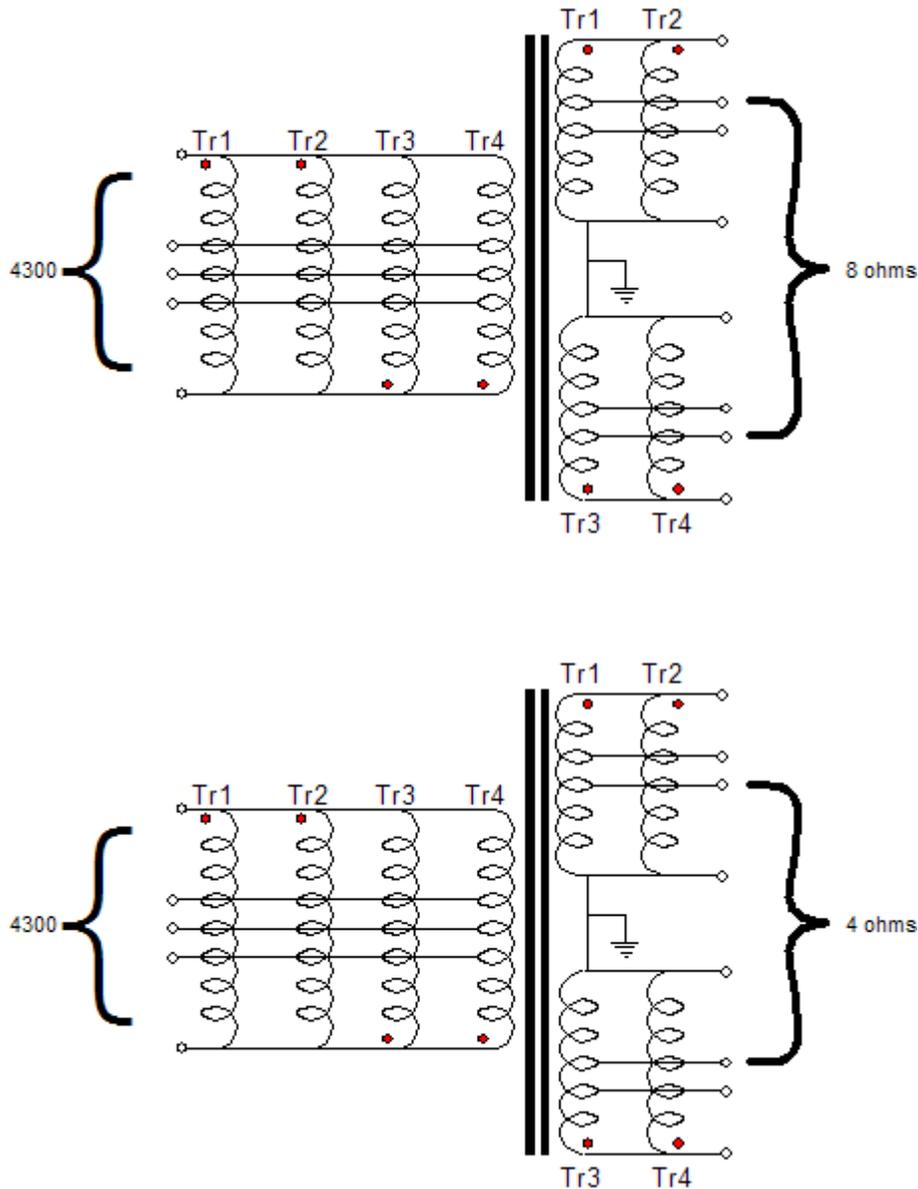
If two transformer's secondaries are placed parallel and then placed in series with another pair placed in parallel, as shown below, the 8-ohm loudspeaker will reflect the desired 1075 ohms and the speaker will see twice the output voltage than one ST-70 would deliver.



Note how the ground connection has been moved to the center. This move has its advantages and disadvantages. On the plus side, we can attach the output tubes' cathodes to the outside ends of our center-tapped secondary, which allows for a simple feedback loop to be realized. On the minus side, more loudspeaker connectors are needed, as we have to reattach both speaker leads, when we

Part	Value	Part	Value	Part	Value	Part	Value
Capacitor	1.5uF MKP	Resistor	10k	Tube	6BD6	Tube	6BD6
Diode	1N4001	Tube	6X4	Tube	6X4	Tube	6X4
Resistor	480 10C	Tube	6X4	Tube	6X4	Tube	6X4
Resistor	10k	Tube	6X4	Tube	6X4	Tube	6X4
Tube	6BD6	Tube	6X4	Tube	6X4	Tube </tr	

Part Type	Name	Quantity	Brand	Vendor
Capacitor	1.5uF MKP	4	Vishay	Essey
Resistor	10k	25	Shals	Essey
Tube	2A3	3	BGA	Electronic Flea Market
Tube	6BD6	7	Ampex	Electronic Flea Market
Tube	6BD7	4	Sylvania	Swag Street
Tube	6BD7	4	Sylvania	Jark's TV Repair
Tube	6BD7	3	Ampex	Flea Market
Tube	6DL7	11	Tung-Sol	Jark's TV Repair
Tube	6DL7	3	Defenestron	Flea Market
Tube	6DL7	15	Sylvania	Flea Market
Tube	12AT7	22	National	Swag Street
Tube	12AT7	11	Ampex	Swag Street
Resistor	10k	8	Variety	Electronic Flea Market
Resistor	4800 ohm	13	Variety	Parts Connection
Tube	6BD7	5	Tung-Sol	Swag Street
Tube	6BD7A	4	GE	Antique Electronic Supply
Tube	6BD7	3	BGA	Swag Street
Tube	6BD7	5	Mullard	Swag Street
Socket	PCB Socket	100	T	Essey

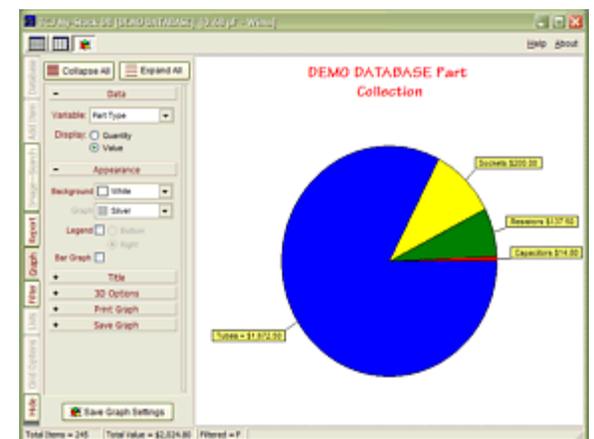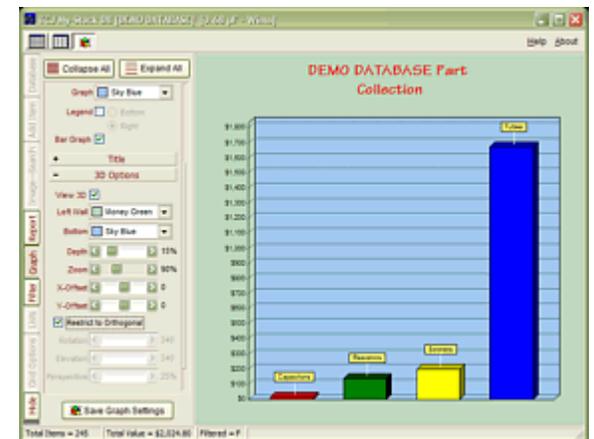


change the speaker's impedance. (Most loudspeakers are either 4 or 8 ohm in impedance, so only four connectors are actually needed in most situations.) Also note how transformers Tr3 and Tr4 have their primaries flipped relative to transformers Tr1 and Tr2. This is necessary to compensate for their secondaries being flipped relative to the other secondaries.

Design example: two Dynaco ST-70s

What if you only own two Dynaco ST-70s? This time the desired reflected impedance is 2150 ohms and the solution is fairly straightforward. We start by placing two output transformers in parallel, both the primaries and secondaries. Next, we re-label the secondary taps; the 16-ohm tap becomes the 8-ohm tap; the 8-ohm tap, the 4-ohm tap; and the 4-ohm tap, the 2-ohm tap. Now each impedance load will see 1.414 times the voltage that a single ST-70 would deliver. (What I like about this arrangement is that none of the secondary is left flapping in the wind when an 8-ohm load is used.)

More pictures

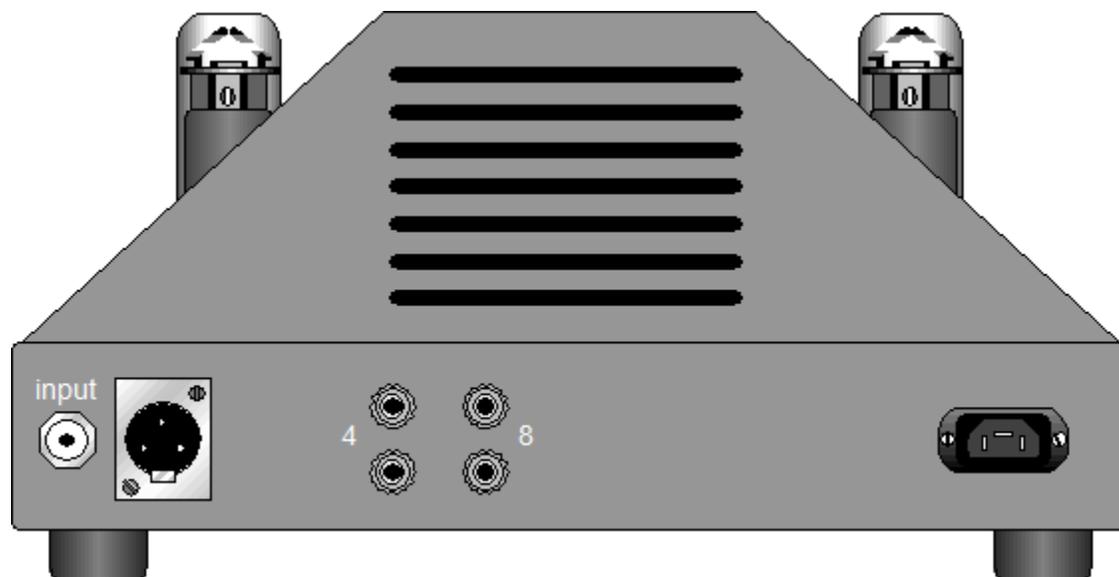Here are more design concept images of what two Dynaco ST-70s would look like as a 140 watt monoblock.



Part Type	Name	Quantity	Brand	Vendor	Electronic Part
Tube	2A3	3	8CA	Electronic Part	
Tube	6SL7	4	Sylvania	Swap Me	
Tube	6807	4	Sylvania	Jays Tr Co	
Tube	6SL7	11	Tung-Sol	Jays Tr Co	
Tube	6SL7	3	Defarreston	Free Mark	
Tube	6SL7	10	Sylvania	Free Mark	
Tube	12AT7	20	National	Swap Me	
Tube	6BD7	5	Tung-Sol	Swap Me	
Tube	588PXA	4	GE	Antique Electron	
Tube	5891	3	8CA	Swap Me	
Tube	6L6	5	Mullard	Swap Me	

TCJ My-Stock DB helps you know just what you have, what it looks like, where it is, what it will be used for, and what it's worth. TCJ My-Stock DB helps you to keep track of your heap of electronic parts. More details.

Version 2 Improvements

- List all of your parts in one DB.
- Add part Images.
- One-click web searches for information.
- Vertical and horizontal grids.*
- Create reports as PDFs.*
- Graphs added 2D/3D: pie & bar.*
- More powerful DB search.
- Help system added.
- Editable drop-down lists for location, projects, brands, styles, vendors and more.


*User definable

**Download or CD ROM
Windows 95/98/Me/NT/2000/XP**


For more information, please visit:

www.glass-ware.com

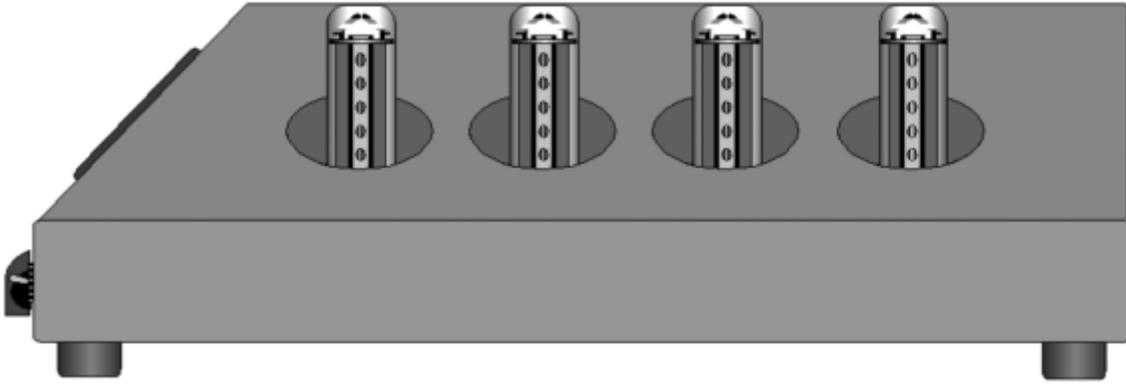
To purchase , please visit our Yahoo Store:
<http://store.yahoo.com/glass-ware>



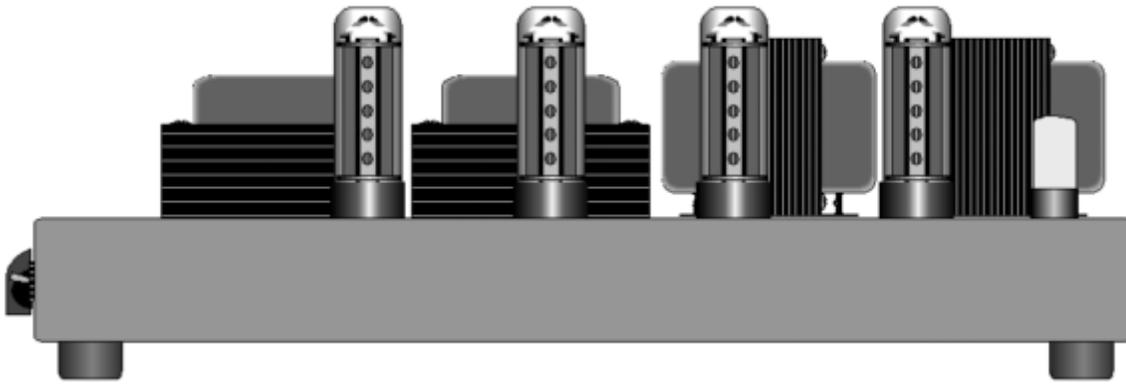[Click on above image to see enlargement](#)



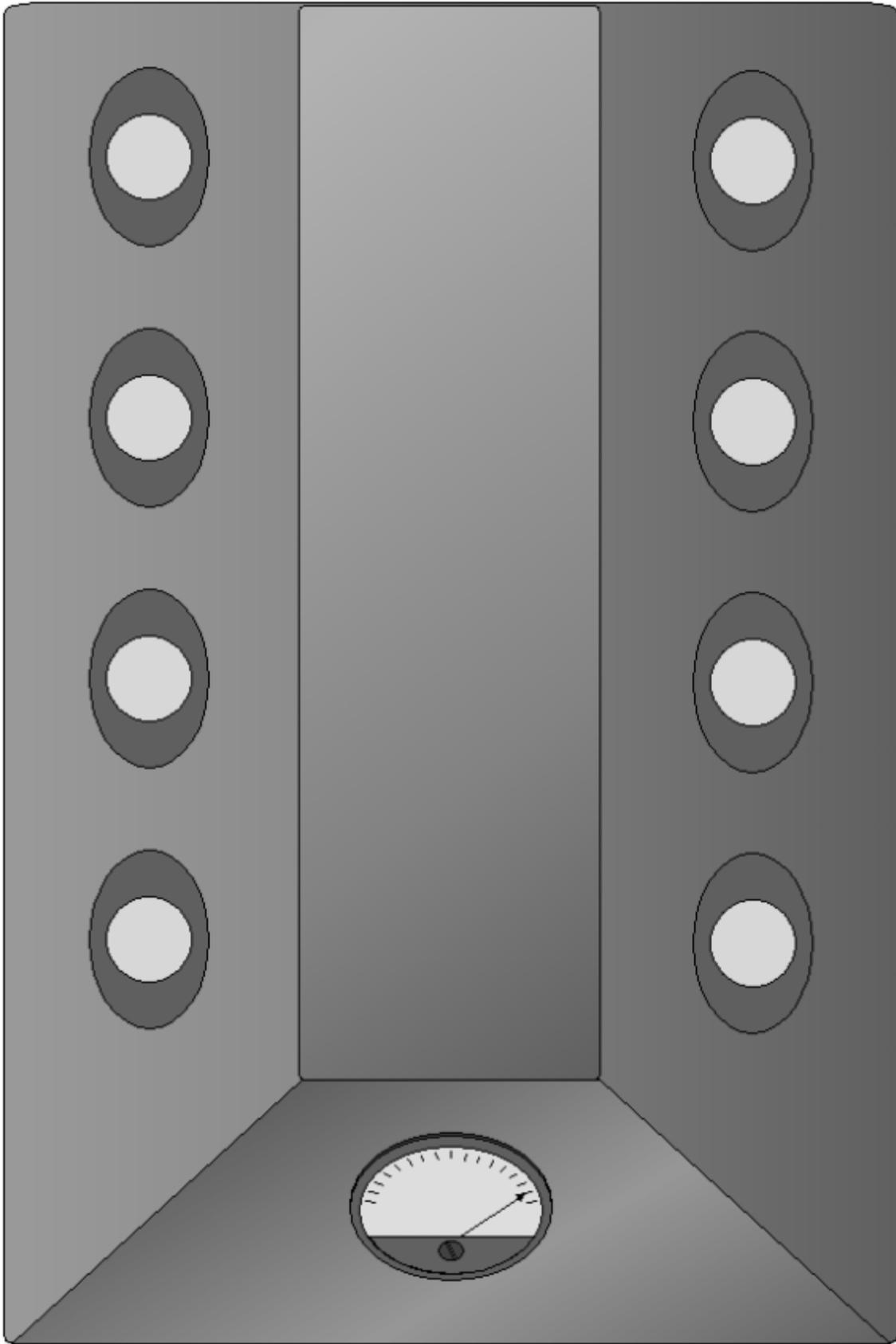[Click on above image to see enlargement](#)



//JRB

[< Back](#)

www.tubecad.com

Copyright © 1999-2005 GlassWare

All Rights Reserved

[Next >](#)