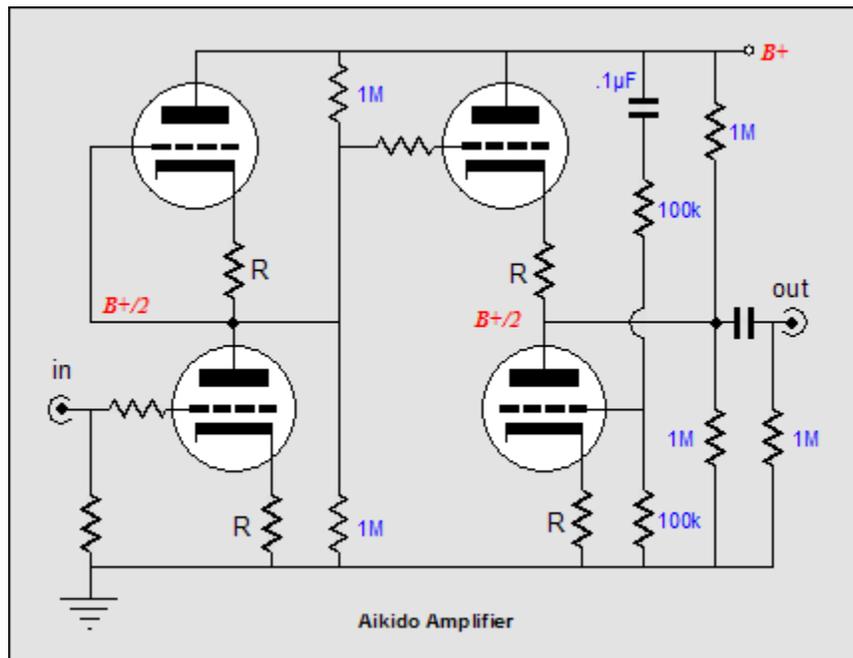


15 July 2005



Aikido Amplifier

Aikido amplifier

Before returning to cathode-follower output stages, a few words on the Aikido amplifier. First of all, this topology is proving to be a big hit, as all the enthusiastic e-mails attest. This makes sense, as the topology provides low distortion and a high PSRR figure. Some, however, undervalue the last attribute, dismissing low noise as the least important aspect of good sound, while proclaiming drive, liquidity, and tone as being much more important. Unfortunately, they miss the point: their desired qualities require that the power supply not undermine an amplifier's attempt to deliver drive or liquidity or tone. (No, I haven't a clue what "drive" is thought to represent; nor, do I believe that you can find more than two audiophiles who would agree on the word's definition—basically, "drive" means what ever you want it to mean, which explains its popularity.)

Support the Tube CAD Journal

&




get an extremely powerful push-pull tube-amplifier simulator for

Only \$29

TCJ Push-Pull Calculator

Version 2

Click on images to see enlargements

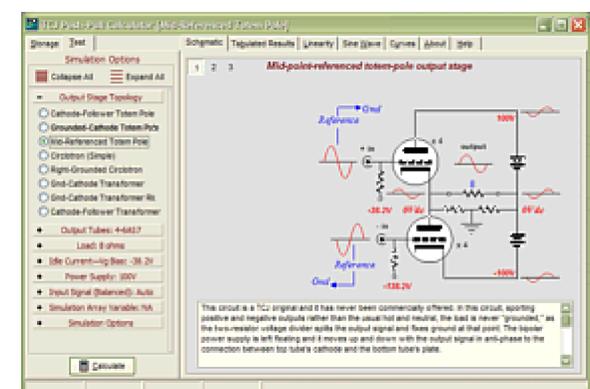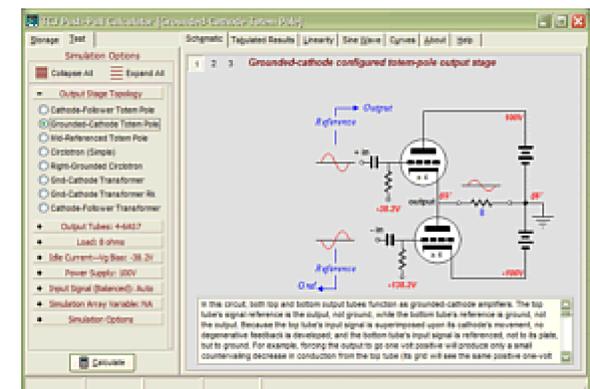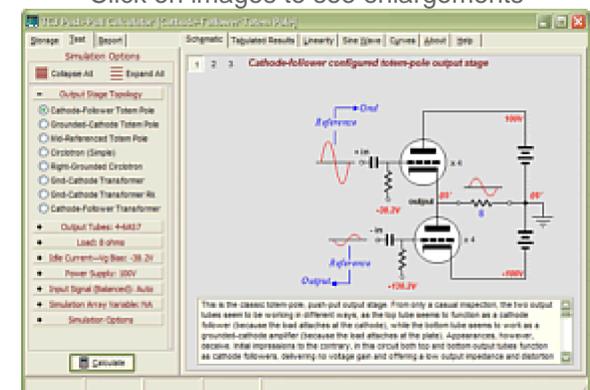








Here's an analogy: you have a great interest in water-color paintings and you hold that the paint's hue and saturation are all important and that those who claim a perfectly white canvas is of primary importance as it will allow the true colors to remain true are clueless technocrats. A good PSRR figure means that the amplifier is able to work around the power supply's imperfections—main frequency hum and rectifier ripple are only two possible power supply failings. The power supply can pollute in more than just these two ways; it can re-circulate the signal from the output stage back into the input and driver stages and then back again... And it may fail to work as intended at only low or only high frequencies, by deviating from being low impedance to being high impedance, any of which may occur in the absence of hum or ripple. The Aikido circuit sidesteps the power supply failings by including them in its normal operation.

Additionally, the Aikido circuit symmetrically balances imperfect triodes against equally imperfect triodes, which greatly reduces its distortion output. The result of these two features is an effortless and natural sound that is hard to improve upon.

In general, I have been trying to paint in broad brushstrokes in this journal. Paradoxically enough, this journal seem to have two types of readers: those who are utter tube novices and those who are complete tube—priests, cardinals, bishops, popes—which best describes some one who, if required, could recreate on his own great chunks of the *Radiotron Designer's Handbook*? Why so few in the middle? My guess is that these audio sophomores simply know all there is to know already, whereas the beginner realizes that he knows little and the expert realizes that, in reality, very little is known by anyone. Thus, my broad brush strokes: those who are starting out will not get lost in long equations and those more accomplished can derive the equations on their own. (Besides, for many, the whole point of tube audio is that it supposedly falls out of the scope of analytic reasoning, being more like magic than engineering.)

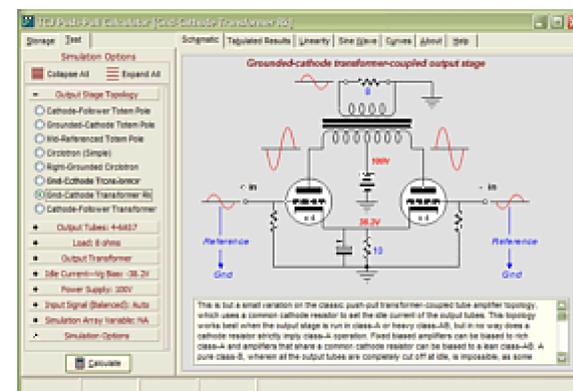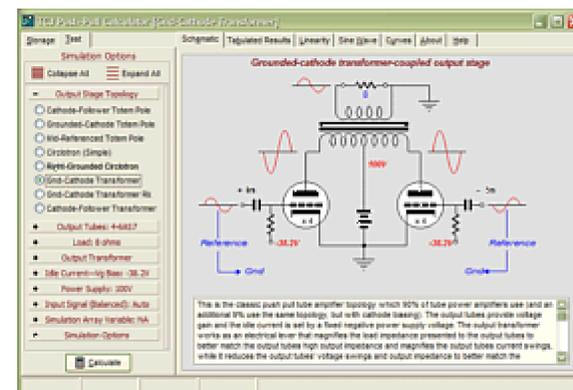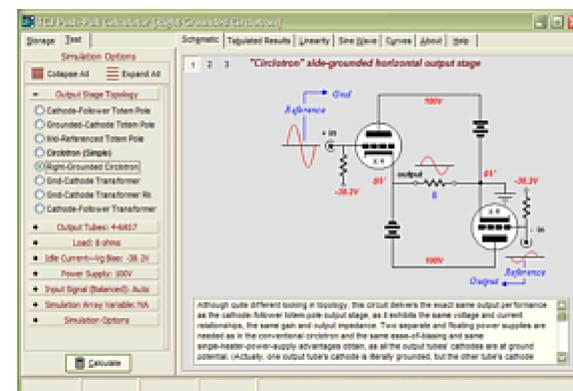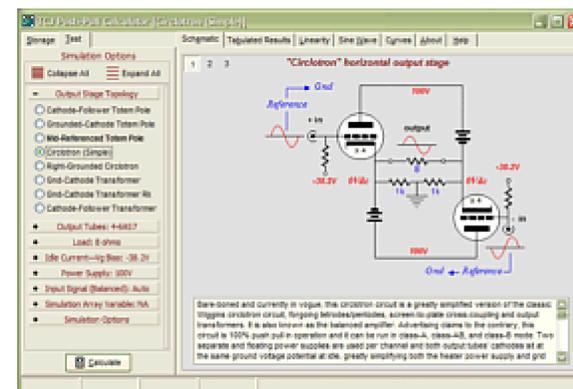However, I believe the Aikido circuit needs a bit finer stroke now that it seems more familiar. The broad-stroke explanation of the Aikido amplifier was that the circuit eliminated power-supply noise from the output, by injecting the same amount of power-supply noise into the top and bottom of the two-tube cathode



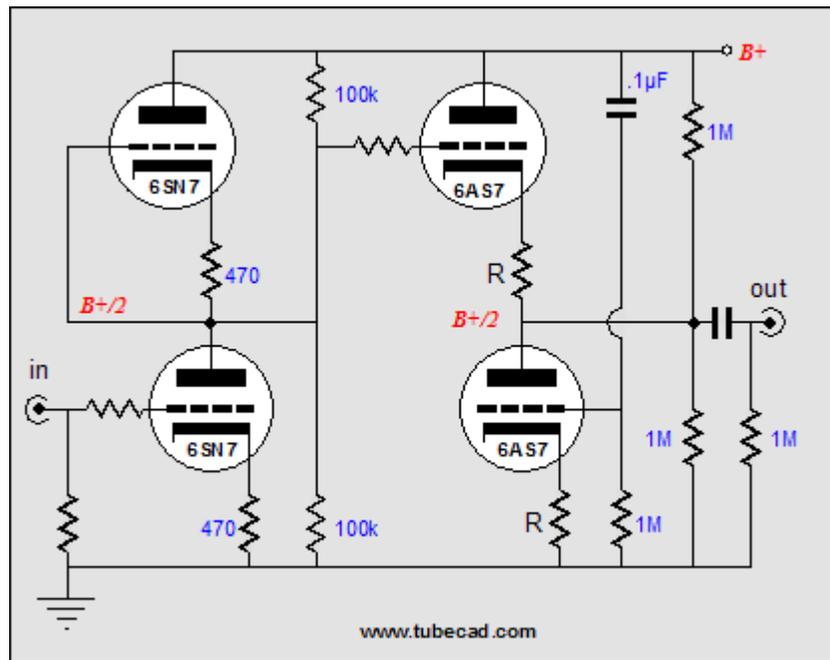

Notice the missing voltage divider; all of the power supply is presented to the bottom triode's grid.




A 6BX7, with a mu of 10, would require a ratio of 60%, which could be made from 40k and 60k resistors in series. A reader from Genova University in Italy, Federico, e-mailed a nice formula for specifying the bottom resistor's value, once the top resistor's value has been established:

$$R_{\text{bottom}} = R_{\text{top}} \times (\mu + 2) / (\mu - 2)$$

Another fine brush detail in the Aikido amplifier's explanation is the role the safety resistors play. In the circuit at the top of the page, the two 1M resistors serve two purposes: the first is to protect the output stage from having the input stage tube pulled from the circuit by providing the same B+/2 voltage to the output stage's top triode's grid. The second purpose is to help burn some gain without penalty. Extra loading on a triode usually only adds distortion, but not in this circuit. Because the top and bottom input stage triodes are equally burdened, the Symmetry God smiles upon the Aikido amplifier. In fact, at least in SPICE simulations, choosing the right resistor values can even lower the distortion of the Aikido amplifier. By specifying the right valued resistors, a sizable decrease in distortion can be realized (a "realized simulation," an interesting description). However, here's the problem with trying for too much in SPICE: the tube models stink and they are perfect. They do not resemble actual tubes and the models are perfectly matched, which real tubes are not. Still, if you can get a -60dB improvement in SPICE, you can probably get an easy -20dB improvement in reality.

Printed circuit boards for the Aikido amplifier

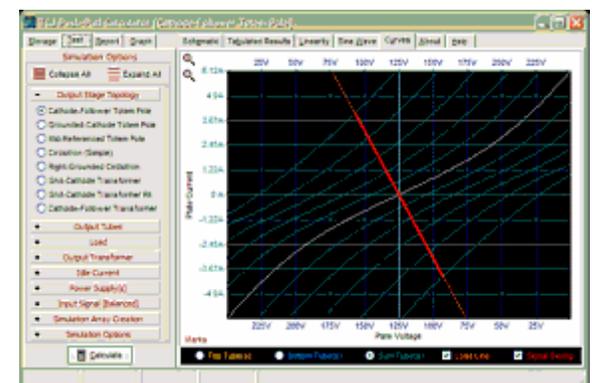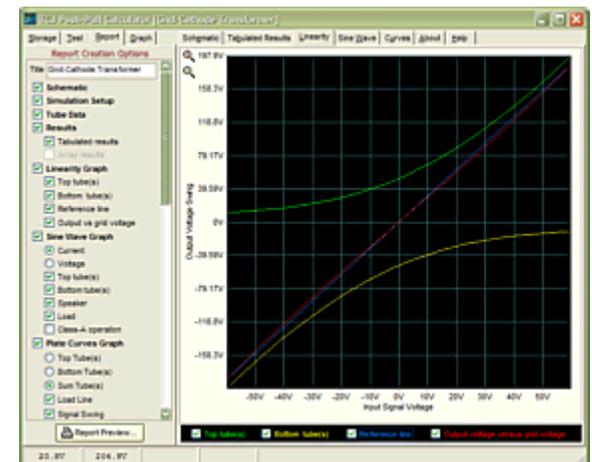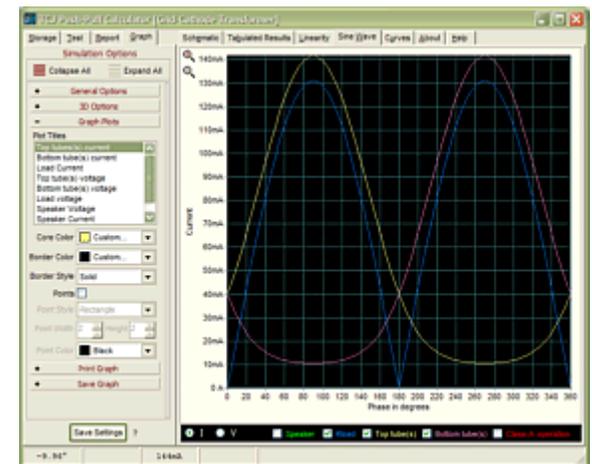Because the interest is so great in the Aikido amplifier, I have been asked if I could provide PCBs to make the circuit easier to build. I looked into having some boards made and the result was that it the more the merrier—and cheaper! How many of



TCJ PPC Version 2 Improvements

- Rebuilt simulation engine*
- Create reports as PDFs**
- More Graphs 2D/3D**
- Help system added*
- Target idle current feature*
- Redesigned array creation*
- Transformer primary & secondary*
- RDC inclusion*
- Save user-defined transformer definitions*
- Enhanced result display*
- Added array result grid*

you readers would like to buy a PCB for the Aikido amplifier? How many did take to save Sodom and Gomorrah? Well, we'll probably need more. Send me an e-mail with Aikido PCB as the subject and let me know how many PCBs you'll need (assuming one per channel); also let me know if you prefer octals or 9-pin miniatures. If the numbers add up, we could be soldering boards in a few weeks.

Next time

Well, it looks like I used up all of my free time just on the Aikido amplifier. Next time, I will present several ways to extract more of the cathode follower's potential as an output stage topology.

//JRB

*User definable

TCJ Push-Pull Calculator has but a single purpose: to evaluate tube-based output stages by simulating eight topologies' (five OTL and three transformer-coupled) actual performance with a specified tube, power supply and bias voltage, and load impedance. The accuracy of the simulation depends on the accuracy of the tube models used and the tube math model is the same True Curves™ model used in GlassWare's SE Amp CAD and Live Curves programs, which is far more accurate than the usual SPICE tube model.

**Download or CD ROM
Windows 95/98/Me/NT/2000/XP**

For more information, please visit our Web site :

www.glass-ware.com

**To purchase, please visit our Yahoo Store:
<http://store.yahoo.com/glass-ware>**

[< Back](#)

www.tubecad.com

Copyright © 1999-2005 GlassWare

All Rights Reserved

[Next >](#)